

End Semester Examination of Semester-I, 2017

Subject : BCA

Paper : BCA-103

Full Marks : 70

Time : 3 Hrs

*The figures in the margin indicate the marks
corresponding to the question*

*Candidates are requested to give their answers
in their own word as far as practicable.*

Illustrate the answers wherever necessary.

Group A

1. Answer **any five** out of eight questions: 2x5=10
- i) Implement EX-NOR gate using NAND Gate.
 - ii) What is the number of flip-flops required for a MOD-10 ring counter?
 - iii) Define parallel and serial registers.
 - iv) What is totem-pole arrangement?
 - v) Difference between Analog and Digital system.
 - vi) What is Race condition? How you resolve it.
 - vii) Write the advantages and disadvantages of K-Map.
 - viii) Draw the circuit of the following Expression $y = A + B + C + D + E + F$ use only 2-input OR gate.

Group B

Answer **any five** out of seven questions : 5×4=20

2. How do you cascade two 2-to-4 decoders to make one 3-to-8 decoder? Draw the necessary circuit.
3. Explain briefly the characteristics of MOS logic and CMOS logic.
4. Design a SR flip-flop with the help of JK flip-flop.
5. Implement one bit full adder using 8-to-1 multiplexers (MUX).
6. i) Convert DF/F to TF/F
ii) What is toggling? 2+2
7. Draw the circuit and shortly explain the operation of 4 bit up-ripple counter.
8. What is DTL logic? Write it's characteristics.

Group C

Answer **any four** out of six questions: 10×4=40

9. a) Draw the basic diagram of a RTL NOR gate. What are the characteristics of the RTL family? 5
b) What is CMOS NAND gate? Draw the basic connection and explain its operation. 5
10. a) Draw the circuit diagram and explain the operation of TTL 3-input NAND gate. 5
b) Implement the following functions using multiplexer $F(A, B, C) = \Sigma(1, 3, 5, 6)$. 5

11. a) Draw and explain the operation of a 5-bit ring counter using JK flip flops. 8
- b) Explain how a flip flop can store a data bit. 2
12. i) Design a 4x2 priority Encoder circuit, having highest priority D3. What is Encoder? 4+1
- ii) Write the differences between decoder and demuxy-circuit. 3
- iii) Find the r's and (r-1)'s complement of $(735)_8$ 2
13. Design AND, OR, NOT, EX-OR and NAND gate using suitable MUX. 2x5
14. i) Draw a 4-bit adder-subtractor circuit and explain it with proper example.
- ii) Write the differences between dual and complement.
- iii) Convert J-K F/F to T F/F. 4+3+3
-